

Hands-On Lab - Module 3 : Results

Your Name: _____ Seat _____ Date _____

CAPACITORS

CHARGING A CAPACITOR

3.1.a) Voltage across capacitor $V_C@τ$ after **one Tau** = 10 seconds;


$$V_C@τ = \text{_____} \text{ volts}$$

3.1.b) Voltage across capacitor $V_C@5τ$ after **five Tau** = 50 seconds;

$$V_C@5τ = \text{_____} \text{ volts}$$

3.1.c) Record the unregulated voltage V (after at least two minutes)

$$V = \text{_____} \text{ volts}$$

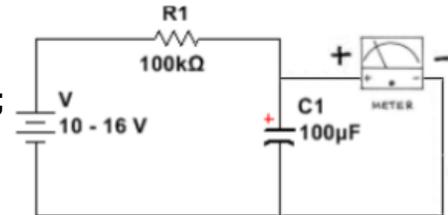

Measured Versus Theoretical Values:

The theoretical capacitor voltage after $one\tau$ should be $\approx 63\%$ of supply voltage V .

3.1.d) Calculate your *actual One Tau* voltage % at 10 seconds:

$$[V_C@τ / V] \times 100\% = \text{Result @ } τ \text{ _____ } \%$$

The theoretical capacitor voltage after $five\tau$ should be $\approx 99\%$ of the supply voltage V .

3.1.e) Calculate your *actual Five Tau* voltage % at 50 seconds;

$$[V_C@5τ / V] \times 100\% = \text{Result @ } 5τ \text{ _____ } \%$$

DISCHARGING A CAPACITOR

3.2.a) How long does it take to discharge the capacitor to **3.7 volts** when connected only to the $1\text{ M}\Omega$ Multimeter? _____ seconds.

(If you do not reach 3.7 volts after about 2 minutes there is an error.)


3.2.b) What is your measured value of $V_C@τ$ after **one Tau** with $100\text{K}\Omega$

and Multimeter ($1\text{M}\Omega$) in parallel (**Requiv** $\approx 90\text{K}\Omega$) ?

$$V_C@τ = \text{_____} \text{ volts}$$

3.2.c) What voltage did you find for $V_C@5τ$ after five Tau?

$$V_C@5τ = \text{_____} \text{ volts}$$

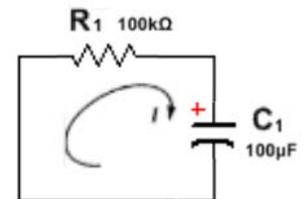


This is Instructor check point 2B.

MEASURING THE CURRENT GAIN OF A TRANSISTOR

3.3.a) Turn the power **ON** and use the **10Kohm** pot knob to adjust the voltage from **0** to full unregulated supply voltage.

Did this work? (___ YES ___ NO)

If this doesn't work ask for help NOW.

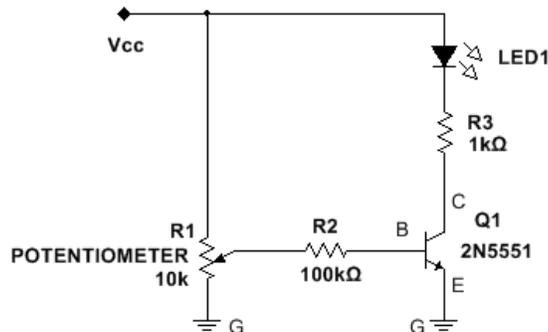

3.3.b) Using the **10Kohm** pot knob to adjust the voltage available to the 100K resistor in the transistor's base circuit it should be possible to vary the brightness of the LED in the collector circuit. Did this work ? (___ YES ___ NO)

TAKING THE MEASUREMENTS

3.4a) Measure the **voltage V_{R2}** across **R_2** (the **100Kohm** resistor connected to the base). The voltage **V_{R2}** is: _____ volts (measured).

3.4b) Measure **V_{BE}** – the voltage from point **B** (base) to point **E** (emitter) – note as the emitter is at ground, The voltage **V_{BE}** is: _____ volts (measured).

3.4c) Calculate the base current using Ohm's Law: **$I_B =$** _____ **mA**
(Calculate using Ohms Law [$I = V/R$] - Remember that **volts / Kohms = mA**)

3.4d) Knowing the collector and base currents, calculate the current gain **$h_{FE} = (I_C / I_B)$**
 $h_{FE} =$ _____ (a number without units)

Fill in Table 3.1 with the appropriate values for the transistor with a 5 ma collector current.

Instructor check point 3C.

3.4e, f) Adjust the **10Kohm** pot to set **V_{R3}** to be **2.0 volts** across **R_3** . Measure the voltage across **R_2** , and then measure **V_{BE}** and fill in the second line of Table 3.1. Repeat for **V_{R3}** equals **1.0 volts**) and then calculate the currents and gains.

I_C	V_{R2}	I_B (mA) = $V_{R2} / 100K$	V_{BE}	$h_{FE} = I_C / I_B$
5 mA				
2 mA				
1 mA				

Table 3.1

Final check:

BEFORE you break the circuit apart, please have your instructor review your setup for the last data set of measurements.