


MSCI 222C – Fall 2021
Introduction to Electronics

Charles Rubenstein, Ph. D.
 Professor of Engineering & Information Science

Session 4: Tues 09/28/2021
 Tuesdays 5:00-7:50pm

Online – Revision 2



Not Permitted in Class



Be sure to have all cellphones **OFF**
 (unless used as calculator...)
Although NOT required
 please turn on your cameras

Copyright © 2021 C.P.Rubenstein 2

21 Fall Class Roster : 222C-01 (TUES 5pm)

MSCI222C – 01 Intro to Electronics

Last Name	First Name	Call Me	Time Zone
Bhargava	Mehul	MEHUL	ET
Briggs	Darius	DARIUS	ET
Chen	Yian	YIAN	ET
Ferreris	Angelica	ANGIE	ET
Gomez	Vladimir	VLADDY	ET
Li	Xiaokun	BROOK	" +12"
Lin	Zili	ZILI	ET
Nam	Hae Ji	LYLA	" +13"
Park	Dong Jun	GEORGE	ET
Tolentino	Lenard Christian	LENARD	ET
Yu	Qim	GLORIA	" +12"
Zhong	Hankiao	HAN	" +12"
Zhou	Amy	AMY	ET

Copyright © 2021 C.P.Rubenstein 3

Instructor Contact Information

Dr. Charles Rubenstein <crubens@pratt.edu>
 Professor of Engineering & Information Science
Brooklyn Campus Faculty Office: ARC G-49

Fall 2021 VIRTUAL Office hours ONLY
 Thursdays: **10:00am - 1:00pm Via Zoom**
Meeting ID: 569 176 2059
Passcode: Office

To make your appointment Send me an email at least one day in advance:
crubens@pratt.edu
Subject line: 222 Office Hour

Copyright © 2021 C.P.Rubenstein 4

US Citizens – Student Alert!

To vote in November you must register. Contact dkahn@nypirg.org



Register & VOTE!

Copyright © 2021 C.P.Rubenstein 5

MSCI 222C – Fall 2021 - ONLINE Schedule

TUESDAY	NOTES
31 August (1)	Session 1. Introduction, Review of Syllabus, Basic Concepts
7 September	NO CLASSES – Instructor’s Religious Holiday
14 September (2)	Session 2. Basic Electronic Devices (Homework #1 Due)
21 September (3)	Session 3. Semiconductor Materials & Semiconductor Diodes (H2, R1)
28 September (4)	Session 4. Transistors as Switches and Amplifiers (H3, R2, L1) Paper Topic Due
5 October (5)	Session 5. Analog and Digital Concepts (H4, R3, L2)
12 October	NO CLASSES – PRATT FALL BREAK
19 October (6)	Session 6. The Operational Amplifier (H5, R4, L3) Midterm Draft Paper Due
26 October (7)	Session 7. Digital Integrated Circuit Logic Gates (H6, R5, L4) Paper Returned
2 November (8)	Session 8. Flip-Flops & "Clocks" (H7, R6, L5) Midterm Exam – 10/31
9 November (9)	Session 9. Digital Counters (H8, R7, L6) Exam Reviewed
16 November (10)	Session 10. Digital Shift Registers (H9, R8, L7)
23 November (11)	Session 11. Using Analog & Digital ICs Together (H10, R9, L8) Final Paper Due
30 November (12)	Session 12. Interfacing Computers and Embedded Devices (R10, L9) Paper Returned
7 December (13)	Session 13. Review of Coding Basics and RFID Concepts (L10) Paper Due
14 December (14)	Session 14. - FINAL Exam

**NOTE: Class is ONLINE – delay in setting up homework quizzes on Canvas...
 Quizzes one week after homework session reviewed
 Labs 1 through 5 are electronics measurement labs.
 Beginning with Session 9 – Arduino Labs with Instruction/IDE Installation, etc.**

Copyright © 2021 C.P.Rubenstein 6

MSCI 222C – Class Readings Schedule	
Session	Readings
2	EW1: Pp 1 - 27; Armstrong: Chapters 1 - 3
3	EW1: Pp 28 - 65; Armstrong: Chapters 4 - 6
4	EW1: Pp 66 - 76; Armstrong: Chapters 7 - 9
5	EW1: Pp 77 -End; Armstrong: Chapters 10 - 11
6	EW2: Pp 1 - 50 and Page 90; Armstrong: Chapters 12 - 13
7	EW2: Pp 51 - 79, Review Page 12; Armstrong: Chapters 14 - End
8	EW2: Pp 80 - End, Review Page 12 (CD4013, CD4017)
9	EW2: Review Page 12 (CD4013, CD4017)
10	EW2: Review Page 37 (555 Timer)
11	Review EW1 and EW2 as necessary, Sensors Lab Manual – if interested
12 and on	Review EW1 and EW2 as necessary

KEY	EW1 = Basic Electronics: Transistors and Integrated Circuits, Workbook 1 by Forrest M. Mims, III (ew1.pdf)
	EW2 = Digital Electronic Projects, Workbook 11 by Forrest M. Mims, III (ew2.pdf)
	Armstrong = Man of High Fidelity (armstrong2.pdf)
	Sensors = Radio Shack Electronic Sensors Lab by Forrest M. Mims, III (sensors.pdf)

Copyright © 2021 C.P.Rubenstein 7

In Today's Class: Session #4

DUE: Research Paper Topic;
DUE: Homework Set #03* (Quiz #03)
Readings: Electronics Workbook 1 (ew1.pdf); Pp 66-76
 Armstrong: Chapters 7-9
Lecture: Transistor Switches and Amplifiers
Reviewed: Homework Set #02
To Do: Pick up Learning Kit (Meter plus Envelope) Next Week!

Assignments now DUE by 12:00Noon ET MONDAYS!!!

For our next class – Session Five:
DUE: Homework Set #04* (Quiz #04)
Readings: Electronics Workbook 1 (ew1.pdf); Pp 77-end
 Armstrong: Chapters 10-11
Lecture: Analog and Digital Concepts
Reviewed: Homework Set #02
To Do: Hands-on Module #01: Measuring Resistance and Voltage

(*) NOTE: Filenames must be lastname_hwk0#.docx, etc.)

Copyright © 2021 C.P.Rubenstein 8

Class Session Archives

www.CharlesRubenstein.com/222

TermPaper.pdf
Info on your Term Paper

Photo2Doc_Process.pdf
How to convert photo into doc file

21fa04.pdf (this slide set)*
21fa04_h.pdf (slide set as handouts)*

**Available by Thursday evenings...*

Copyright © 2021 C.P.Rubenstein 9

Revised MSCI 222C Hands-on Lab Modules

#01: Measuring Resistance and Voltage
#02: Voltage Sources, LEDs, Diodes & Characteristic Curves

NEW VERSIONS OF THESE AS WELL AS ARDUINO LABS:
#03: Capacitors, Time Constants & Transistor Gain
#04: Voltage Regulation & Transistor Switching
#05: Analog IC Voltage Comparator
#06: Basic Digital Logic
#07: Set-Reset Latches & Type "D" Flip-Flops
#08: Decade Counter and 'One Shot' Switch Debouncer
#09: NE555 IC Timer Circuits
#10: Seven Segment Display Decoder-Driver Circuit
Arduino Labs #1 through #?

Copyright © 2021 C.P.Rubenstein 10

Questions?

Copyright © 2021 C.P.Rubenstein 11

IV. Supplemental Materials

The Pratt Electronics Learning Kit

The kit contains a Digital Multimeter and special leads, a power supply, and an Arduino Basic Startup Kit.

If you are local to Pratt you will be instructed when/where to pick up your kit.

If you are outside of the US...

We have other arrangements which have been emailed to you which review what you need to do to get reimbursed for a kit for your hands-on lab modules.

Please try to obtain these LOCALLY so you can begin the lab by end of September.

Copyright © 2021 C.P.Rubenstein 12

The Pratt Electronics Learning Kit

Pick up your Electronics Learning Kit NEXT WEEK in ARC G-39

Name of Item	US\$ Cost	Part URL:
Digital Multimeter	6.99	https://www.harborfreight.com/7-function-digital-multimeter-63759.html
Hi-Lego Red/Black 4MM Banana Plug to Test Hook Clip Test Lead (3 pairs - you only receive ONE)	7.39	https://www.amazon.com/dp/B073SP3G6D
ELEGOO UNO Project BASIC Starter Kit	17.99	https://www.amazon.com/dp/B01DGID2GAO
9VDC @ 1Amp Power adapter	6.99	https://www.amazon.com/dp/B01S0LREG4
JBtek Breadboard Power Supply Module 3.3V/5V	6.99	https://www.amazon.com/dp/B010UJFVTU

Copyright © 2021 C.P.Rubenstein 13

The Elegoo Arduino Starter Kit

EL-KIT-004 Elegoo Arduino Basic Starter Kit Component listing:

- UNO R3 Controller Board and USB Cable
- 1pcs Breadboard
- 1pcs 65 Jumper Wires and 5pcs Female-to-male DuPont Wire
- 1pcs 74HC595 (8-bit Serial IN, Parallel OUT Latching Shift Register Integrated Circuit)
- 1pcs EACH: Active Buzzer and Tilt Switch
- 1pcs Photoresistor
- 5pcs EACH: Red, Yellow, Green, Blue and White LEDs
- 1pcs RGB LED
- 5pcs SPST Button (small)
- 10pcs Resistor (10R = 10 Ω)
- 10pcs Resistor (100R = 100 Ω)
- 10pcs Resistor (220R = 220 Ω)
- 10pcs Resistor (330R = 330 Ω)
- 10pcs Resistor (1K = 1,000 Ω)
- 10pcs Resistor (2K = 2,000 Ω)
- 10pcs Resistor (5K1 = 5,100 Ω)
- 10pcs Resistor (10K = 10,000 Ω)
- 10pcs Resistor (100K = 100,000 Ω)
- 10pcs Resistor (1M = 1,000,000 Ω)

Copyright © 2021 C.P.Rubenstein 14

Questions?

Copyright © 2021 C.P.Rubenstein 15

V. Method of Assessment & Grading

Hands-on Lab Work	40% (4% each)
Ten Homework Quizzes	20% (2% each)
MidTerm Exam	10%
Research Papers:	
MidTerm Review of Paper	10%
<i>(Proposal 5%; Draft 5%)</i>	
Final Paper	20%
<i>(Draft 5%, Final Paper 10%, Bibliography 5%)</i>	

Copyright © 2021 C.P.Rubenstein 16

Submitting Your Assignments

Homework Set #XX as well as all other submissions are due to me, via email, not later than 12:00pm Noon ET **MONDAY** the day before class.

The filename for homework submissions is:
lastname_hwkXX.doc or lastname_hwkXX.docx or lastname_hwkXX.pdf

The filename for the Midterm Exam is:
lastname_midterm.doc (etc.)

The filename for the various Paper submissions is:
lastname_topic.doc (etc.)

NOTE: *If you are creating hand-written pages as a picture, please see the instructions on the next page and in the file: Photo2Doc_Processing.pdf*

Copyright © 2021 C.P.Rubenstein 17

V.a. Hands-On Labs

Hands-on Lab Work 40% (4% EACH)

Hands-on work involves actually wiring of working electronic circuits without soldering. The hands-on work score is based on completion of the hands-on work opportunities.

Student grades are not downgraded for requesting help, so if try 2 or 3 or 4 works - full credit is earned.

There are ten (10) **REQUIRED** and up to two (2) **OPTIONAL** labs.
Optional Labs are worth an additional 5% each!

Also see **POLICIES** in the Syllabus.

Special Note:
Lab work will ONLY be accepted up to the week before the last week of classes

Copyright © 2021 C.P.Rubenstein 18

V.b. Homework, Quizzes & Midterm

Homework Quizzes 20%

HOMEWORK IS DUE NOT LATER THAN 12:00Noon ET ON THE MONDAY BEFORE OUR CLASS SESSION

There will be a Quiz on one homework problem worth 2%

Homework quizzes count for 20% of your final grade.

- Homework assignments **MUST** be emailed to me not later than 12:00pmNoon ET the **MONDAY** before our class.
- I will grade one question on the week's homework as a 'quiz'.
- Homeworks will be reviewed the week they are due, **thus if NOT emailed to me, they will receive a grade of 0%.**

NOTE: There are no make up quizzes or exams.

Copyright © 2021 C.P.Rubenstein

19

About the Midterm Exam

Two hour Midterm Exam (10%)

This will be an Exam on electronics theory and common calculations in analog electronics – similar to homework – covering Ohm's Law, voltage dividers, power, resistors, diodes, transistors, etc., emailed to all not later than **9:00am ET on Sunday 31 October** and due back to me by email not later than **1:00pm ET** on that same day.

NOTE: These will be the Same DUE date/times for BOTH US and International Students

The filename for the Midterm Exam is:

lastname_midterm.doc or lastname_midterm.docx or lastname_midterm.pdf

Copyright © 2021 C.P.Rubenstein

20

V.c. Midterm Research Paper (10%)

This is a term paper on an electronic component, device or system you are interested in.

The DRAFT 'midterm' paper consists of:

1. 3-page Draft paper.
2. PLUS one additional bibliography page - with **four or more** references.

DEADLINE (Due not later than 12:00pmNoon ET **MONDAYS**)

- Proposed Paper Topic Paragraph Due (5%): **9/28**
- 3-page Midterm Draft Paper Due (5%): **10/18**
- Returned with my Comments: **10/25**

The filename for the various Paper submissions is: **lastname_topic.doc (rtf, docx, etc.)**

Copyright © 2021 C.P.Rubenstein

21

21 Fall Term Paper Topics

MSCI222C – 01 Intro to Electronics

As of 12:00pm Noon ET 28 September

Last Name	First Name	Call Me	Topic
Bhargava	Mehul	MEHUL	Resistors
Briggs	Darius	DARIUS	AM and FM Radio
Chen	Yian	YIAN	3D Printers/Augmented Reality
Ferreris	Angelica	ANGIE	NFTs
Gomez	Vladimir	VLADDY	Elektrosluch 3+
Li	Xiaokun	BROOK	Yet Not Submitted
Lin	Zili	ZILI	Temperature Sensors
Nam	Haee Ji	LYLA	Interactive Sensors
Park	Dong Jun	GEORGE	Virtual Reality
Tolentino	Lenard Christian	LENARD	LED Strips
Yu	Quin	GLORIA	Controlling LEDs
Zhong	Hansiao	HAN	Ohm's Law
Zhou	Amy	AMY	Transistors

Copyright © 2021 C.P.Rubenstein

22

V.d. Final Research Paper (20%)

This is a **continuation** of your midterm paper.

The **SIX (6)** page draft paper final materials consist of:

1. Revised and expanded Midterm Paper
2. Plus a bibliography page - with **four or more** references - **NOT** included in the page count above.

DEADLINE (Due not later than 12:00pmNoon ET **MONDAYS**)

- 6-page Final Paper Draft Due (5%): **11/22**
- Returned with my Comments: **11/29**
- Final Paper Due: **12/6**

(Final Paper 10%, Bibliography Page 5%)

The filename for the various Paper submissions is:

lastname_Draft.doc (docx, rtf, etc.) or lastname_Final.doc (docx, rtf, etc.)

Copyright © 2021 C.P.Rubenstein

23

Questions?

Copyright © 2021 C.P.Rubenstein

24

MSCI 222C Electronics Review

The basics are essential


Ohms Law
eMath Calculations
Combining Resistors
Voltage Divider Equation

Copyright © 2021 C.P.Rubenstein 25


Ohms Law

There are three forms for the Ohms Law equation:

$V = I R$
 $R = V / I$
 $I = V / R$




and a convenient figure to remember it by...



Copyright © 2021 C.P.Rubenstein 26

About Electronics Math Calculations...

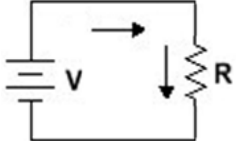Ohms Law equation: $V=IR$
 and $I = V / R$




1. If R is **1 Ohm** = 1 Ω and V is **1 volt**:
 then $I = 1 \text{ Ampere}$
2. If R is **1MΩ** = 1,000,000 Ω and V is **1 volt**:
 then $I = 1 \text{ microampere} = (1 \mu A = 1 \mu A)$
3. If R is **1k Ohm** = 1kΩ = 1000Ω and V is **1 volt**:
 then $I = 1 \text{ milliampere} (= 1 \text{ mA})$

This is the most common calculation for our labs...

Copyright © 2021 C.P.Rubenstein 27


Series Resistors: REVIEW

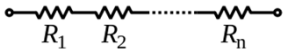

1. Resistors in **SERIES** add
 $R_{ab} = R_1 + R_2 + \dots + R_n$
2. For 'n' Like Resistors in **SERIES**:
 $R_{ab} = n \cdot R$

Copyright © 2021 C.P.Rubenstein 28


Parallel Resistors: REVIEW

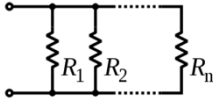

1. The Inverse of Resistances in **PARALLEL** add
 $1/R_{ab} = 1/R_1 + 1/R_2 + \dots + 1/R_n$
2. For **TWO** Resistors in Parallel;
 $R_{ab} = R_1 R_2 / (R_1 + R_2)$
3. For 'n' Equal Resistances in Parallel;
 $R_{ab} = R / n$

Copyright © 2021 C.P.Rubenstein 29

Simple Series/Parallel Resistor Circuits

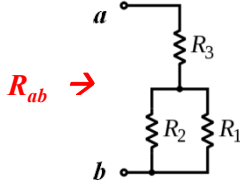


The Equivalent Resistance of the circuit above:

$R_{ab} = [R_1 R_2 / (R_1 + R_2)] + R_3$

Copyright © 2021 C.P.Rubenstein 30

The Voltage Divider Equation

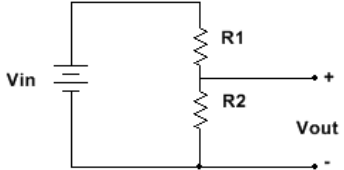


The Voltage Divider Equation
 $V_{out} = V_{in} [R_2 / (R_1 + R_2)]$

When a voltage is applied to two (or more) resistors in series, the voltage across a particular resistor is the applied voltage times the selected resistor, divided by the sum of the resistors

Copyright © 2021 C.P.Rubenstein 31

Kirchhoff's First Law: KCL, the Current Law

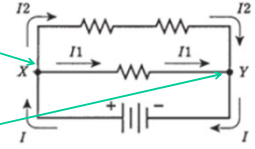KCL: Kirchhoff's First Law
 We call X and Y 'nodes.'
 Kirchhoff noted that *the current into node X (or node Y) is the same as the current out of that node:*



KCL@ node x:
 $I = I_1 + I_2$


KCL@ node y:
 $I_1 + I_2 = I$

Copyright © 2021 C.P.Rubenstein 32

Kirchhoff's Second Law: KVL, the Voltage Law

Consider what you already learned about *series circuits*:
 The *voltages across* all the individual resistors (R_1, R_2, R_3, R_4) add up to the supply voltage. **BUT** the polarities of the EMFs across the resistors are opposite to that of the battery.

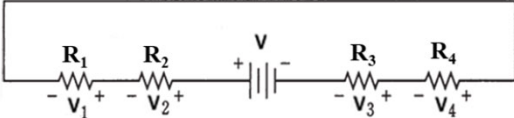It becomes clear when a series circuit is drawn with all the components, including the battery source, in line with each other:




The sum of all the voltage rises and voltage drops = zero
KVL $\rightarrow (-V_1) + (-V_2) + V + (-V_3) + (-V_4) = 0$

Copyright © 2021 C.P.Rubenstein 33

Capacitors in Parallel

Although we will **not** go through the mathematics at this time, note that the capacitor symbol shows two separated plates.

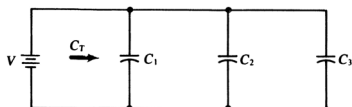
It makes sense then to consider the connection of two or more capacitors in **PARALLEL** would yield more plate area and thus it makes sense that **Capacitor Values in Parallel ADD**
(in the same way resistors add in series):



$C_T = C_1 + C_2 + C_3$

Copyright © 2021 C.P.Rubenstein 34

Capacitors in Series

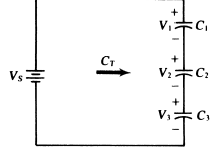

As with resistors in parallel,
 for "n" capacitors in series *their inverses add*:

$1/C_T = 1/C_1 + 1/C_2 + \dots + 1/C_n$


And the equivalent capacitance for "n" *equal valued capacitors* in series is *1/n* times the individual value of capacitance:

$C_T = C_1/n$

Copyright © 2021 C.P.Rubenstein 35

TWO Capacitors in Series

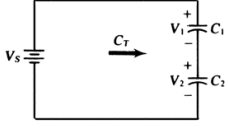Similarly, when capacitors are connected in **SERIES** their voltages add but the current is the same, again, without doing the math, let's accept that **Capacitor values in Series are calculated in the same way as resistors in parallel...**



For two capacitors in series, the product of their values over the sum of their values equals the effective capacitance:

$C_T = (C_1 \cdot C_2) / (C_1 + C_2)$

Copyright © 2021 C.P.Rubenstein 36

τ - Charging a Capacitor

$\tau = R C$

For any given RC combination, after **one Tau (τ)** the capacitor voltage will reach **63% of V** (point a in Figure 11).

After **5 x Tau (5τ)** the capacitor voltage will exceed **99% of V** (point b in Figure 11).

In other words:
a capacitor will be more than half charged in one Tau and for all practical purposes will be seen as fully charged after 5 Tau.

Copyright © 2021 C.P.Rubenstein 37

Discharging Capacitors: Tau (τ)

When a capacitor is initially charged to some voltage $V_{initial}$ and is allowed to discharge into a resistor R , once again $\tau = R C$ controls the timing.

After **one Tau** the capacitor voltage will be down to **37% of Vinitial** (point a at right) and after **5 Tau** it will be less than **1% of Vinitial** (point b at right)

Figures 12. Capacitor Timing When DISCHARGING (into R w/no Voltage source)

The capacitor will be more than half discharged after one Tau and for all practical purposes fully discharged after 5 Tau.

Copyright © 2021 C.P.Rubenstein 38

Time Constant NOTES

The time required to charge or discharge a capacitor requires calculating:

$\tau = R \cdot C$

*With: τ in seconds,
R in ohms, and
C in Farads*

Copyright © 2021 C.P.Rubenstein 39

Forward/Reverse Biasing of Diodes REVIEW

Semiconductor diodes have the ability to pass the flow of current in only one direction. This occurs when the diode is

Forward Biased:

$I_{R1} \approx V / R1$
 $I_{R1} = (V - 0.6) / R1$

Similarly, semiconductor diodes have the ability to block the flow of current in one direction. This occurs when the diode is

Reverse Biased:

$I \approx 0$

Copyright © 2021 C.P.Rubenstein 40

Diode Circuit Problems - 1

Basic Ohms Law Calculation: $R_S = (V_S - V_F) / I_F$

1. What is R_S if $V_S = 5$ and $V_F = 2$ volts @ 10 mA:

$R_S = (V_S - V_F) / I_F$
 $R_S = (5v - 2v) / 10mA$
 $R_S = 3 / 10 \times 10^{-3} = 3 / 0.010 = 300 \text{ ohms}$

2. If $R_S = 100$ ohms, what is I_F :

$R_S = (V_S - V_F) / I_F$ and thus,
 $I_F = (V_S - V_F) / R_S$
 $I_F = (5v - 2v) / 100 = 0.030A = 30mA$

Copyright © 2021 C.P.Rubenstein 41

Diode Circuit Problems - 2

Now consider a three LED Circuit

Once again, using Ohms Law:

$R_S = (V_S - V_{LED}) / I_F$
If $V_F = 1.2$ volts
then $V_{LED} = [3 \times 1.2v]$
and therefore
 $R_S = (V_S - [3.6]) / I_F$
If we knew I_F and V_S
we could calculate R_S

Copyright © 2021 C.P.Rubenstein 42

Questions?

Copyright © 2021 C.P.Rubenstein 43

MSCI 222C Electronics

Homework #02 / Quiz #02

Resistors in Series & Parallel

Average Grade: %
(does not include those NOT submitting their work)

Copyright © 2021 C.P.Rubenstein 44

Homework 2.A Armstrong Questions

Armstrong Reading Questions:

2.A1) What was Armstrong's Mother's maiden name?
Page 7:
Armstrong's Mother's maiden name was *Emily Smith*

2.A2) By 1917, Armstrong was receiving invention royalties of about \$500/month (same buying power as \$10,350/month today!). What circuit was this for?
Page 2:
The royalties were from amateur radio operators using Armstrong's *Regenerative/Feedback Amplifier Circuit*

Copyright © 2021 C.P.Rubenstein 45

Homework 2.B1

2.B1) Find the voltage from a to b (across R_2) in Figure 1, on the right, using the voltage divider equation.

$$V_{R2} = R_2 \cdot (V / [R_1])$$



$$V_{R2} = 4 \text{ ohms} \cdot (30 \text{ volts} / [56+4] \text{ ohms})$$

$$V_{R2} = 4 \cdot (1/2) \text{ volt-ohms} / \text{ohms} = 2 \text{ Volts}$$

Compare HW#2 Figure 1 to HW#1 Figure 4 until it is clear to you why the answer to HW#1.4b must be the same as the answer to HW#2.1 here.

HWK 1 Figure 4 has a 50 ohm and 6 ohm in series with the 4 ohm resistor: 50+6 = 56 ohms!

Thus the circuits are the same with $R_1 + R_2$ of Fig. 4 = R_1 of Fig. 1 above, and R_3 of Fig. 4 = R_2 of Fig. 1

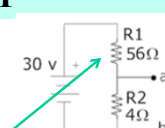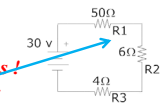Copyright © 2021 C.P.Rubenstein 46

Homework 2.B2

2.B2a) Find the *current* leaving the 30V source in Figure 2, on the right.
(Hint-start by combining the two 20 ohm resistors).

$$R_2 // R_3 = [(R_2 \cdot R_3) / (R_2 + R_3)] = (400/40) = 10 \text{ Ohms}$$

$$R_T = R_1 + [R_2 // R_3] = 50 + 10$$


$$R_T = 60 \text{ Ohms}$$

Using Ohms Law:

$$I_T = V / R_T = 30 \text{ volts} / 60 \text{ Ohms} = 0.5A (= 500 \text{ mA})$$

2.B2b) Now find the voltage from a to b (across R_3)

$$V_{R3} = I_T \cdot [R_2 // R_3] = 0.5A \cdot 10 \text{ ohms}$$

$$V_{R2} = 5 \text{ Volts}$$


Copyright © 2021 C.P.Rubenstein 47

Homework 2.B3

2.B3) Find the voltage from a to b (across R_2) in Figure 3 using the voltage divider equation.

$$V_{R2} = R_2 \cdot (V/R_T)$$



$$V_{R2} = 10 \text{ ohms} \cdot (30 \text{ volts} / [50+10] \text{ ohms})$$

$$V_{R2} = 10 \cdot (1/2)$$

$$V_{R2} = 5 \text{ Volts}$$

Then examine & compare Figures 2 and 3 until it is clear to you why the answer to #2b must be the same as the answer to #3.

Figure 3 is the same as Figure 4 after we combine the two parallel resistors, R_2 and R_3 .

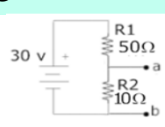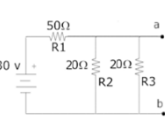Copyright © 2021 C.P.Rubenstein 48

Homework 2.C4

2.C4) Find the power dissipated in a **130 ohm** resistor carrying **60mA** (recall that $1\text{ mA} = 0.001\text{ Amp}$).

Using the Power Law Formula:

$$P = I^2R$$

$$P = (0.060\text{ Amps})^2 \times 130\text{ Ohms}$$

$$P = 0.0036 \times 130$$

$$P = 0.468\text{ Watts} = 468\text{ mW}$$

Copyright © 2021 C.P.Rubenstein 49

Homework 2.C5

2.C5a) (3 Points)
Find the power dissipated in a **100 ohm** resistor carrying **60mA** (recall that $1\text{ mA} = 0.001\text{ Amp}$).

$$P = I^2R = (0.060\text{ Amps})^2 \times 100\text{ Ohms}$$

$$P = 0.0036 \times 100$$

$$P = 0.360\text{ Watts} = 360\text{ mW}$$

2.C5b) (3 Points)
Is this power level within the ratings of a **1/2 watt** resistor?
(Yes, No)

BUT, barely as 50% of power rating = 250 mW, is the preferred maximum value

Copyright © 2021 C.P.Rubenstein 50

Questions?

Copyright © 2021 C.P.Rubenstein 51

MSCI 222C Electronics

Hands-On Lab Module 1: Measuring Resistance and Voltage **POSTPONED UNTIL NEXT WEEK!**

Copyright © 2021 C.P.Rubenstein 52

In Class Session #5

Assignments now DUE by 12:00Noon ET MONDAYS!!!
DUE and Reviewed: Homework Set #04* (Quiz #04)
Readings: Electronics Workbook I (ew1.pdf): Pp 77 - end
 Armstrong: Chapters 10-11
Lecture: Analog and Digital Concepts
Reviewed: Homework Set #03, #04
To Do: Hands-on Module #01: Measuring Resistance and Voltage

12 OCTOBER – MIDTERM BREAK – NO CLASSES

In Session 6:
DUE and Reviewed: Homework Set #05* (Quiz #05); Lab #01
Readings: Electronics Workbook II (ew2.pdf): Pp 1 – 50, Page 90
 Armstrong: Chapters 12-13
Lecture: Operational Amplifier Concepts
To Do: Hands-on Module #02: Voltage Sources, LEDs, Characteristic Curves

NOTE: Hands-on Module #03+: Under Development, to be distributed
 (*) **NOTE:** Filename must be *lastname_hwk0#.docx*, etc.)

Copyright © 2021 C.P.Rubenstein 53

Any Questions? Send me an email ...

crubnst@pratt.edu

Copyright © 2021 C.P.Rubenstein 54

