

READINGS: Electronics Workbook 1 (**ew1.pdf**): Pages 28-65  
 Man of High Fidelity (**armstrong.pdf**): Chapters 4-6

*This assignment is due at the beginning of the next class. There will be a one question quiz on this homework ONE WEEK after the homework is reviewed.*


## 1. Armstrong Reading Questions

- 1.A1)** What was Armstrong's Mother's maiden name?  
**2.A2)** By 1917, What circuit was Armstrong receiving invention royalties of about \$500/month (same buying power as \$10,350/month today!) for?

## 2. Voltage Dividers

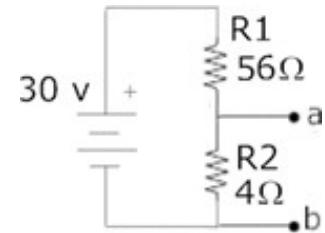- 2.B1)** Find  $V_{ab}$ , the voltage across  $R_2$  from **a** to **b**, in Figure 2.1, on the right, using the voltage divider equation.

*Compare HW#2 Figure 1 to HW#1 Figure 4 until it is clear to you why the answer to HW#1.4b must be the same as the answer to HW#2.1 here.*



- 2.B2a)** Find the **current I** leaving the **30V source** in Figure 2, on the right.

(Hint-start by combining the two **20 ohm** resistors).

- 2.B2b)** Find the voltage  $V_{ab}$  from **a** to **b** (across  $R_3$ ).

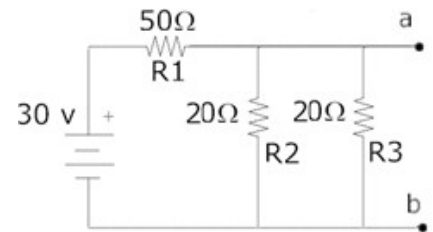


Figure 2.2 Series/Parallel Voltage Divider Circuit

- 2.B3)** Using the voltage divider equation find the voltage  $V_{ab}$  from **a** to **b** (across  $R_2$ ) in Figure 3.

*Then examine and compare Figures 2 and 3 until it is clear to you why the answer to #2b must be the same as the answer to #3.*

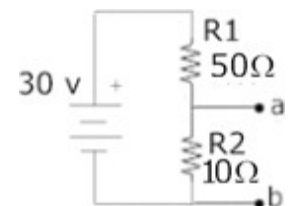


Figure 2.3 Voltage Divider Circuit

## 3. Power Dissipation in Resistors

(NOTE: 1 mA = 0.001 Amp)

- 2.B4)** Find the power dissipated in a **130 ohm** resistor carrying **60mA**

- 2.B5a)** Find the power dissipated in a **100 ohm** resistor carrying **60 mA**.

- 2.B5b)** Is the calculated power level for the 100 ohm resistor within the ratings of a **1/2 watt** resistor? (Yes, No)


*Note: This question presumes the resistor is in an open, well-ventilated, space. If a resistor is used in an enclosed space, e.g. inside a small box, it is good practice not to exceed 50% of the stated power rating.*

#### 4. Charging Capacitors

**4.a.** Consider a capacitor being charged through a resistor from a 16-volt source. (*presume the input voltage is exactly 16 volts*).

**2.B6a)** What is the *approximate theoretical* value of voltage across the capacitor after **one time constant**?

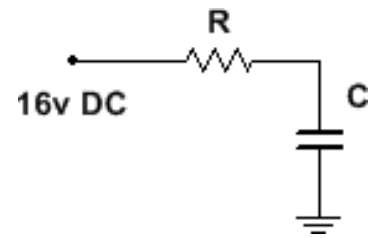**2.B6b)** What is the *approximate theoretical* value of voltage across the capacitor after **5 time constants**?



**4.b.** If a capacitor is charged to exactly **16 volts** and is then **discharged** through a switch into a resistor.

**2.B7a)** What is the *approximate* voltage across the resistor,  $V_R$ , after **one time constant**?

**2.B7b)** What is the *approximate* voltage across the resistor,  $V_R$ , after **5 time constants**?

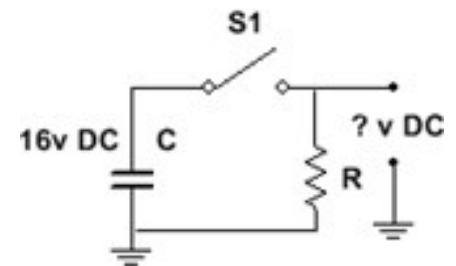


Figure 2.5 Capacitor as Voltage Source Circuit

#### 5. Calculating Time Constants

**2.B8)** With a series resistor of **100K $\Omega$** , what value of capacitance would be required to have a time constant of **1 minute**?

(*Due to current leakage in real electrolytic capacitors, the actual charging times will be slower. Ignore this effect and calculate an approximate, ideal, estimate of the time constant.*)

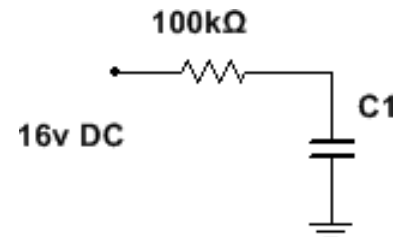


Figure 2.6 RC Time Constant Circuit